

10.2.1 Intermediate amplifier in common cathode-circuit

The standard version of the intermediate amplifier contains *one* tube (almost always a triode) in common-cathode configuration. The circuit is similar or even identical to the first preamp-stage. And why not – the signal has been attenuated by tone-filter and/or volume control and needs to be re-amplified, with the common-cathode configuration being highly suitable. Sometimes, the developers see a need for an impedance conversion in the second amplifier stage – this aspect we will cover in the next section (10.2.2).

In the **common-cathode circuit**, the cathode is connected to “common” i.e. to ground. The required grid-offset is usually generated “automatically” by a cathode-resistor (Chapter 10.1). A capacitor is connected across this resistor in order for the latter to be active only for DC, and to avoid any AC-voltage across it (which would introduce negative feedback). As long as there is not grid-current, this circuit features very high input impedance – although a non-negligible input capacitance (100 pF minimum) does require consideration. The output impedance (internal impedance) results from the parallel connection of the internal impedance of the tube (about 60 k Ω) and the plate-resistor (100 k Ω); the gain factor is about 35 dB (or a bit less if there is significant loading).

Fig. 10.2.2 shows two famous amplifier concepts in comparison: in the Fender circuit, the volume potentiometer directly follows the tone-filter and feeds the intermediate stage, while in the VOX, the intermediate stage is placed between volume pot and tone-filter. **Fender** follows the simple line of thinking: take care of all control efforts at one and the same location. The interaction between the directly connected volume control and tone-filter remains within reasonable limits because the pot is of relatively high impedance (1 M Ω). With the **VOX**, we find an entirely different approach: a special intermediate amplifier with high-impedance input (common cathode configuration) and low-impedance output (common-plate configuration, see 10.2.2) follows the volume pot.

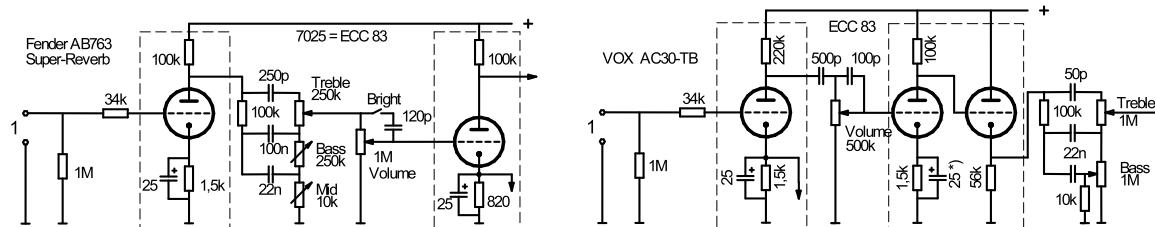


Fig. 10.2.2: Comparison between a typical Fender-circuits (left) and a VOX-circuit (right).

*) There are VOX amps that do not include the cathode-capacitor for the 2nd tube.

Pushing the discussion of the tone-filter into Chapter 10.3, we will first analyze the 2nd tube-stage of the **Fender circuit**. Both 1st and 2nd tube-stages are fundamentally similar but there are differences regarding the cathode circuit: in the Super Reverb (under scrutiny here), the cathode-RC-circuit also feeds the corresponding cathode of a tube in the other input-channel. Other Fender amplifiers include the same component-saving detail. In the figure, the second tube is not included but an arrow indicates the connection to it. For the grid-offset of the tube(s) to remain at the desired value, the value of the cathode-resistor common to both tubes is approximately halved at 820 Ω (instead of 1,5 k Ω). Since both triodes are feeding relatively high impedance circuits, they have similar voltage gains. Given a regular ECC83, each triode will yield about 32 – 34 dB. The harmonic distortion, however, will be different because the source impedances (ahead of the grid) differ.